

Characteristic Curves Tracer for diode, bipolar and field effect transistors with
NI myDAQ

NAZARBAEV UNIVERSITY

ASTANA 2016

ROBT 204 – ELECTRIC AND ELECTRONIC CIRCUITS II

Characteristic Curves Tracer for diode, bipolar and field effect transistors with NI myDAQ

Required Apparatus

- NI myDAQ;
- Diode (N4001), BJT (2N3904), JFET (2N5457);
- OP AMP (LM741CN);
- LabView application for characteristics curve tracer;
- Resistors: 1k Ω , 1M Ω ;
- Digital multimeter;
- Electric component kit;
- Bread board and conductors

Reference textbook

- Course textbook: Electronic Devices and Circuit Theory, R. L. Boylestad, L. Nashelsky

Experiment Objectives

- Measurement of the input and output characteristics of a bipolar junction transistor (BJT).
- Enhance conceptual knowledge about Semiconductor diode, BJT, JFET characteristics and experienced in using NI myDAQ.
- Design and building a circuit for LabView application for NI myDAQ for IO characteristics curve of Semiconductor diode, BJT, JFET.

Report

- Show your obtained results of each step to the instructor or TAs

Introduction

Semiconductor diode

A diode is a two-terminal element, usually made by using a p-n junction (the operation of which is explained in detail in ROBT204 class).

The symbol for a diode is shown in Fig.1 (a). Which terminal is which matters very much in a diode. Usually, the terminal indicated by a horizontal line in Fig. 1 (a), called the cathode, is marked on a real diode; see, for example, Fig. 1(b). We define the voltage (v_D) and the current (i_D) of a diode as shown in the figure. These two quantities are related, as shown in Fig. 1(c). When the voltage v_D is positive, the diode is said to be forward-biased; a large current can then flow, and the diode is said to conduct. When the voltage v_D is negative, the diode is said to be reverse-biased; the diode current is extremely small, and for our purposes it is assumed to be zero; the diode is then said to be turned off. Thus, the diode effectively conducts current in only one direction (downward in Fig. 1); it “refuses” to conduct current in the other direction. This property turns out to be very useful, as you will find out in this experiment.

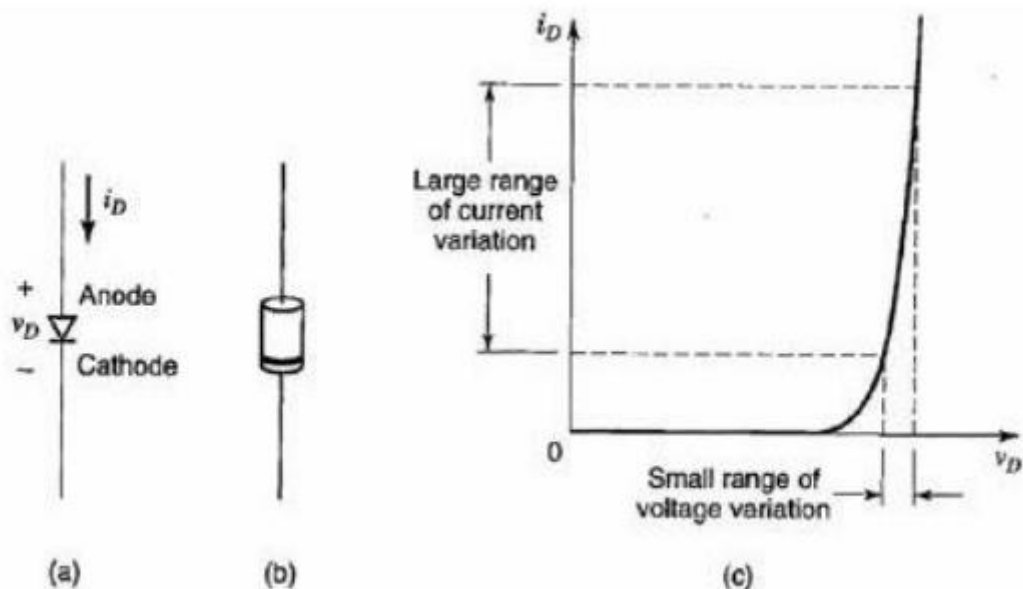


Fig. 1 – Symbolic representation of diodes (a), diode (b), diode characteristic.



1N4001

BJT transistor

Transistors fall into two categories (bipolar junction or bipolar and field-effect) and are also classified according to the semiconductor material employed (commonly silicon, others are germanium, gallium arsenide, etc.) and to their field of application (e.g. general purpose, switching, high frequency, etc.). Various classes of transistor are available according to the application concerned.

Bipolar transistors generally comprise NPN or PNP junctions of either silicon (Si) or germanium (Ge) material. (See Figs. 1 and 2). The junctions are produced in a single slice of silicon by diffusing impurities through a photographically reduced mask (in course Integrated Circuit Design). Germanium devices are rarely encountered and are ignored here. Figures 1 and 2, respectfully, show a simplified representation of NPN and PNP transistors together with circuit symbols.

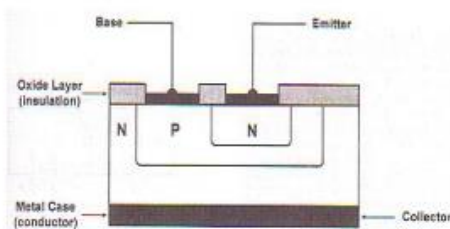


Fig. 1 – NPN transistor construction

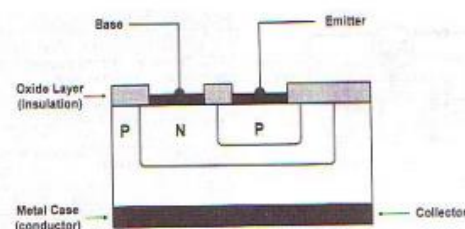


Fig. 2 – PNP transistor construction

In either case the electrodes are labelled collector, base and emitter. Note that each junction within the transistor, whether it be collector-base or base-emitter, constitutes a P-N junction.

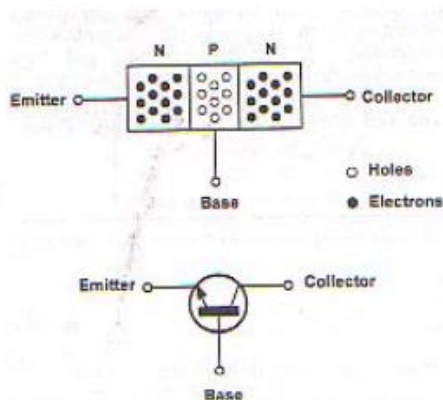


Fig. 3 – Simplified model of an NPN transistor

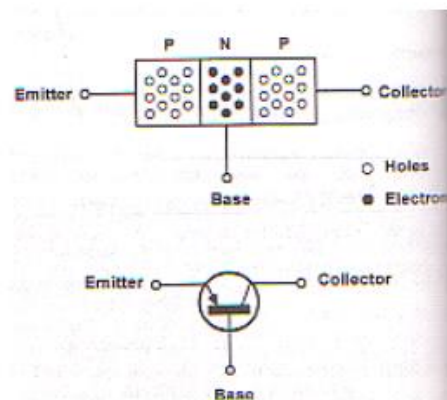


Fig. 4 – Simplified model of a PNP transistor

Two sets of characteristics are again necessary to describe fully the behavior of the common-emitter configuration: one for the input or base-emitter circuit and one for the output or collector-emitter circuit. Both are shown in Fig. 5.

The emitter, collector, and base currents are shown in their actual conventional current direction. Even though the transistor configuration has changed, the current relations developed earlier for the common-base configuration are still applicable. That is, $I_E = I_C + I_B$ and $I_C = \alpha I_E$.

For the common-emitter configuration the output characteristics are a plot of the output current (I_C) versus output voltage (V_{CE}) for a range of values of input current (I_B). The input characteristics are a plot of the input current (I_B) versus the input voltage (V_{BE}) for a range of values of output voltage (V_{CE}).


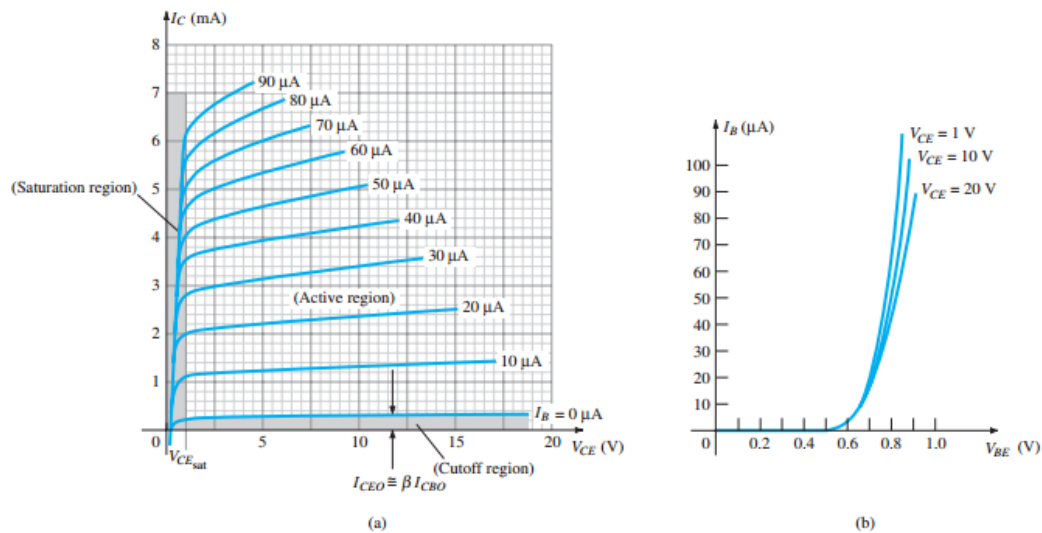


Figure 5: Characteristics of a silicon transistor in the common-emitter configuration: (a) collector characteristics; (b) base characteristics.

Construction and characteristics of JFET

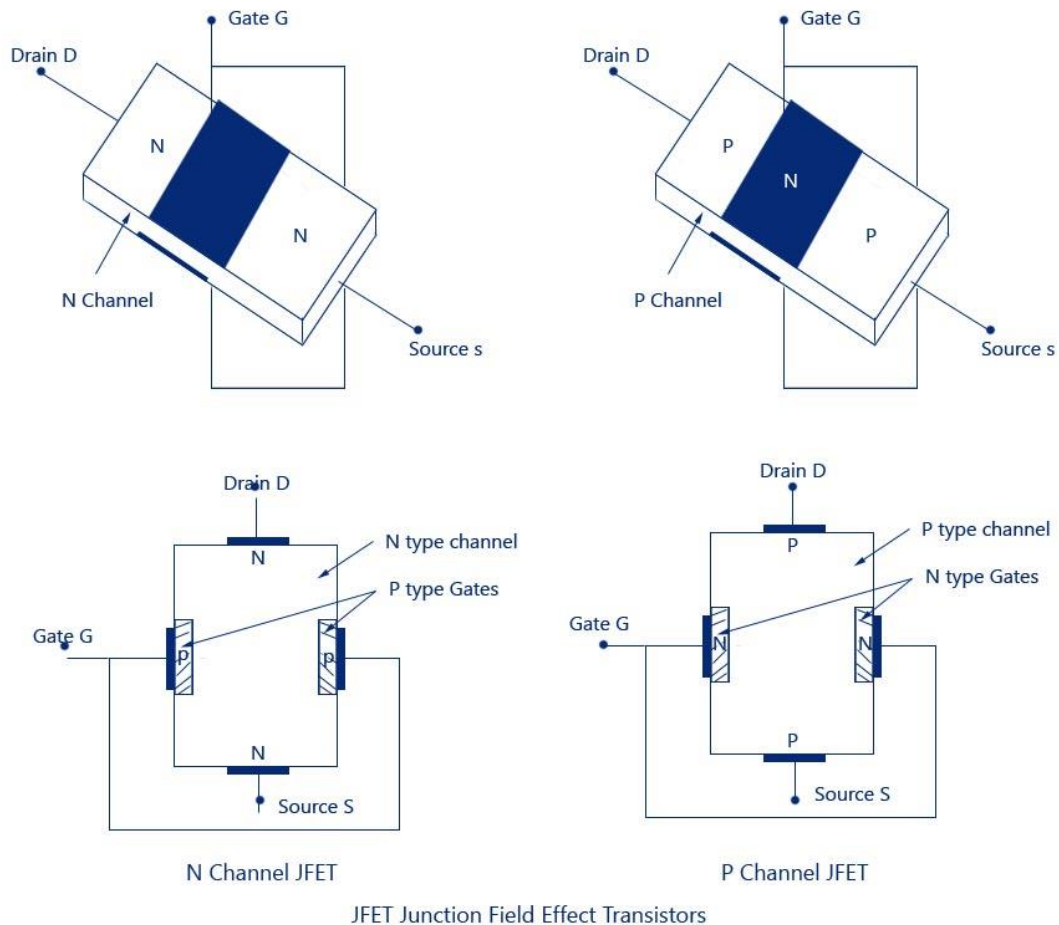JFET's are of two types, namely N-channel JFETs and P-channel JFETs. Generally N-channel JFETs are more preferred than P-channel. N-channel and P-channel JFETs are shown in the figures below.



JFET Junction Field Effect Transistors

Standard Notations in FET:


Source – The terminal through which the majority carriers enter the channel, is called the *source* terminal S and the conventional current entering the channel at S is designated as I_s .

Drain – The terminal, through which the majority carriers leave the channel, is called the *drain* terminal D and the conventional current leaving the channel at D is designated as I_D .

The drain-to-source voltage is called V_{DS} , and is positive if D is more positive than source S

Gate – There are two internally connected heavily doped impurity regions formed by alloying, by diffusion, or by any other method available to create two P-N junctions. These impurity regions are called the gate G. A voltage V_{GS} is applied between the gate and source in the direction to reverse-bias the P-N junction. Conventional current entering the channel at G is designated as I_G .

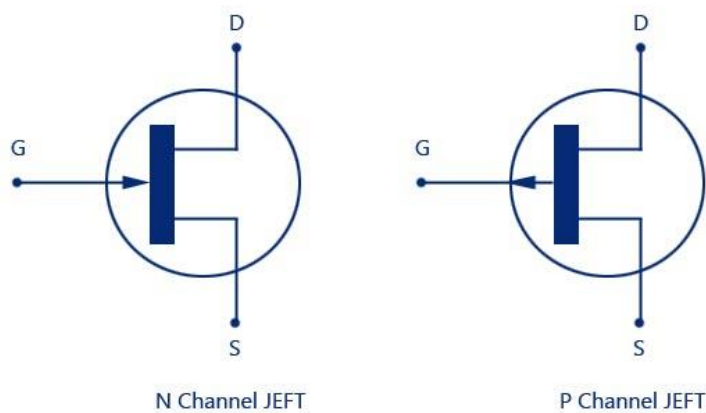Channel – The region between the source and drain, sandwiched between the two gates is called the *channel* and the majority carriers move from source to drain through this channel.



JFET-N-Channel and P-channel Schematic Symbol

The graphical approach, however, will require a plot of Eq.1 to represent the device and a plot of the network equation relating the same variables. The solution is defined by the point of intersection of the two curves. It is important to keep in mind when applying the graphical approach that the device characteristics will be unaffected by the network in which the device is employed.

The network equation may change along with the intersection between the two curves, but the transfer curve defined by Eq. 1 is unaffected. In general, therefore:

The transfer characteristics defined by Shockley's equation are unaffected by the network in which the device is employed.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

↑ constants
 ↑ control variable

Equation 1: Shockley's equation.

The transfer curve can be obtained using Shockley's equation. In Fig. 6 two graphs are provided, with the vertical scaling in milliamperes for each graph. One is a plot of I_D versus V_{DS} , whereas the other is I_D versus V_{GS} . Using the drain characteristics on the right of the “y” axis, we can draw a horizontal line from the saturation region of the curve denoted $V_{GS} = 0$ V to the I_D axis. The resulting current level for both graphs is I_{DSS} . The point of intersection on the I_D versus V_{GS} curve will be as shown since the vertical axis is defined as $V_{GS} = 0$ V.

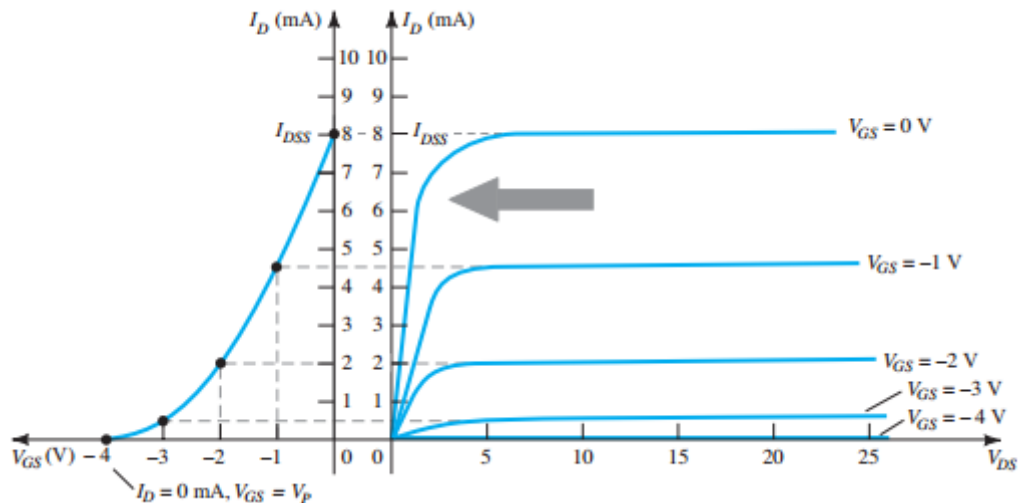


Figure 6: Obtaining the transfer curve from the drain characteristics.

LabView application

In this lab experiment we are going to use application that made on LabView and NI myDAQ tool to trace diode, BJT and JFET characteristics curves. All that we do in this experiment building appropriate circuit, running application and analyzing result. Application itself is LabView program that all necessary codings is already ready to work.

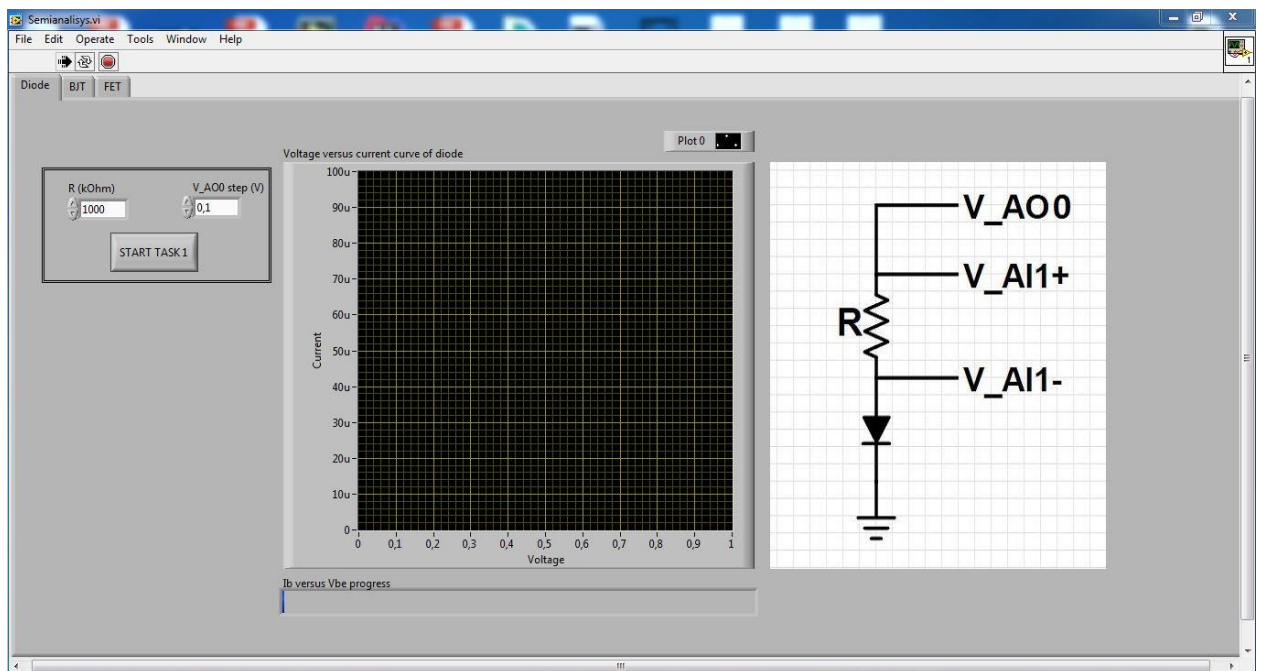


Figure 7. Interface of application

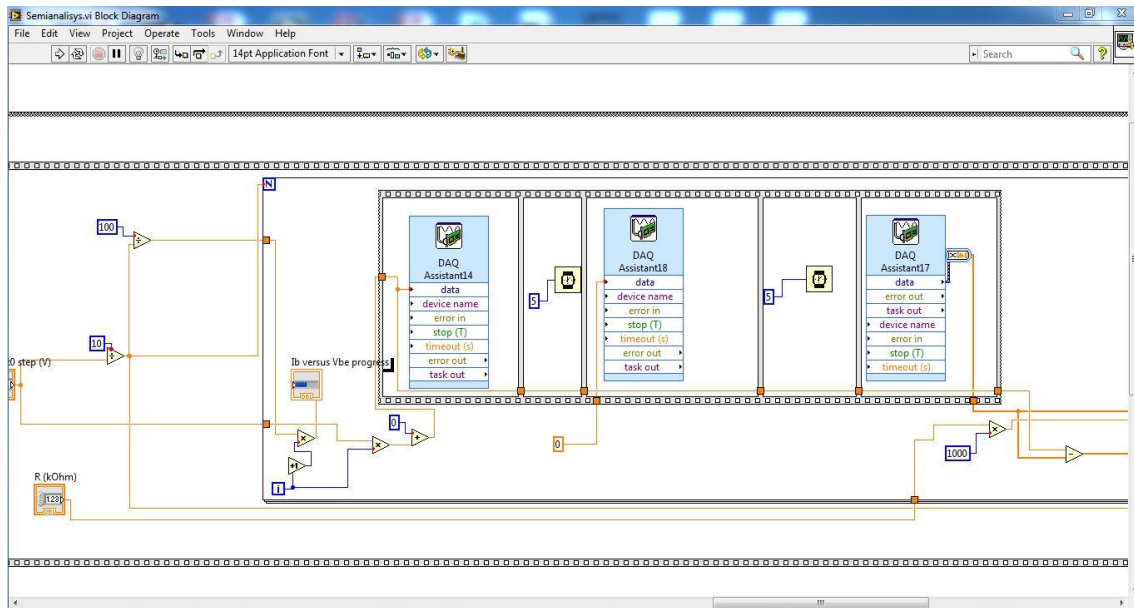


Figure 8. Block diagram of application.

NI myDAQ is a low-cost data acquisition (DAQ) device that gives students the ability to measure and analyze live signals anywhere, anytime. We will use two voltage analog outputs, two voltage analog inputs and constant voltages (+15 V, -15V).

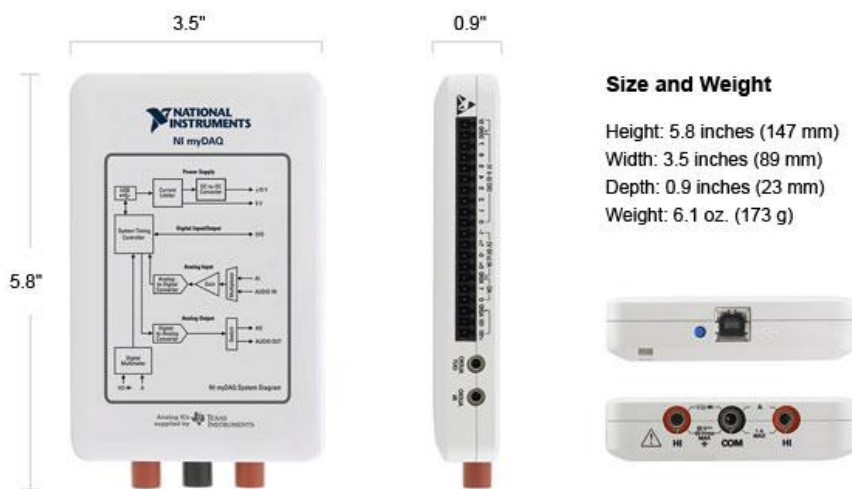


Figure 9. NI myDAQ tool

Application controls NI myDAQ tool to generate and acquire appropriate analog voltages through pins(Fig 9).

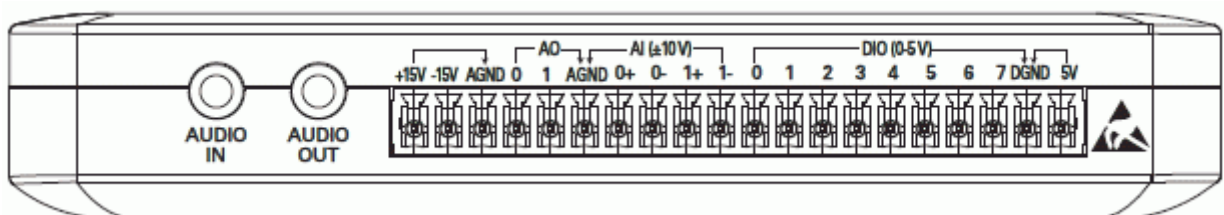


Figure9. NI myDAQ pins.

Task 1

Diode characteristics curve

V_AO 0 will generate analog DC voltage which will be increasing by V_AO 0 step which you write in the application. NI myDAQ will read difference between V_AI 1+ and V_AI 1- and divide by R which is our current through diode. Each iteration will be putted on the graph and make curve.


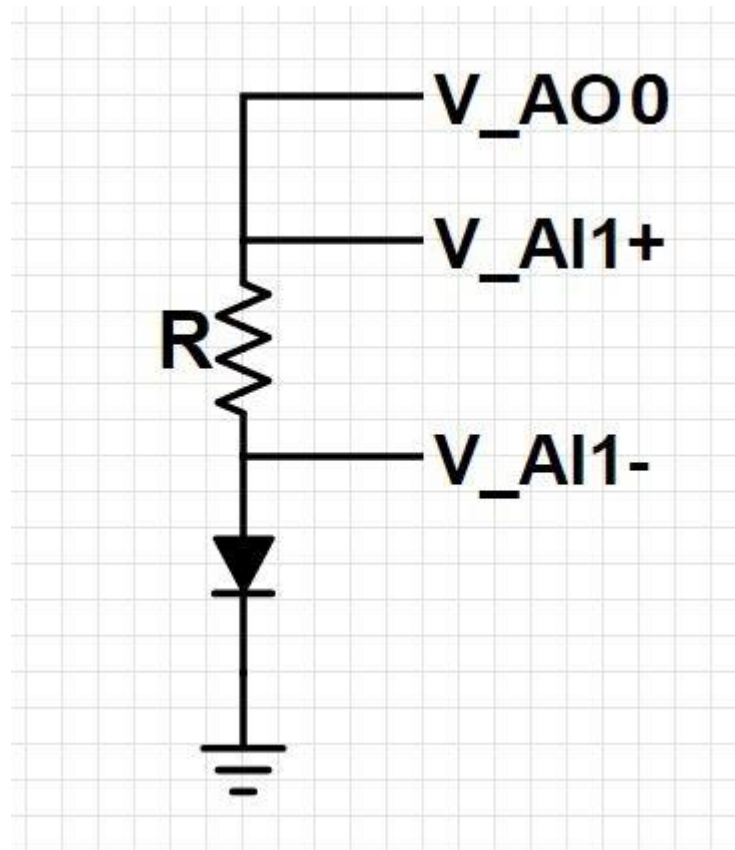



Figure 10. Circuit for analyzing diode characteristics.

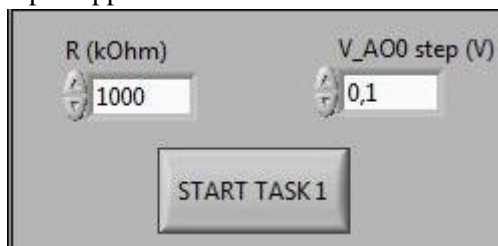1. Build the circuit as shown in Figure 10. $R = 100\text{ k}\Omega$. Silicon diode (1N4001).
2. Connect to correct pins of NI myDAQ . Ground to AGND.
3. Measure resistor by using digital multimeter.
4. Open application and write founded value of resistor to R and put 0.1 V for V_AO 0 step



5. Run application

6. Finally you should have something like this

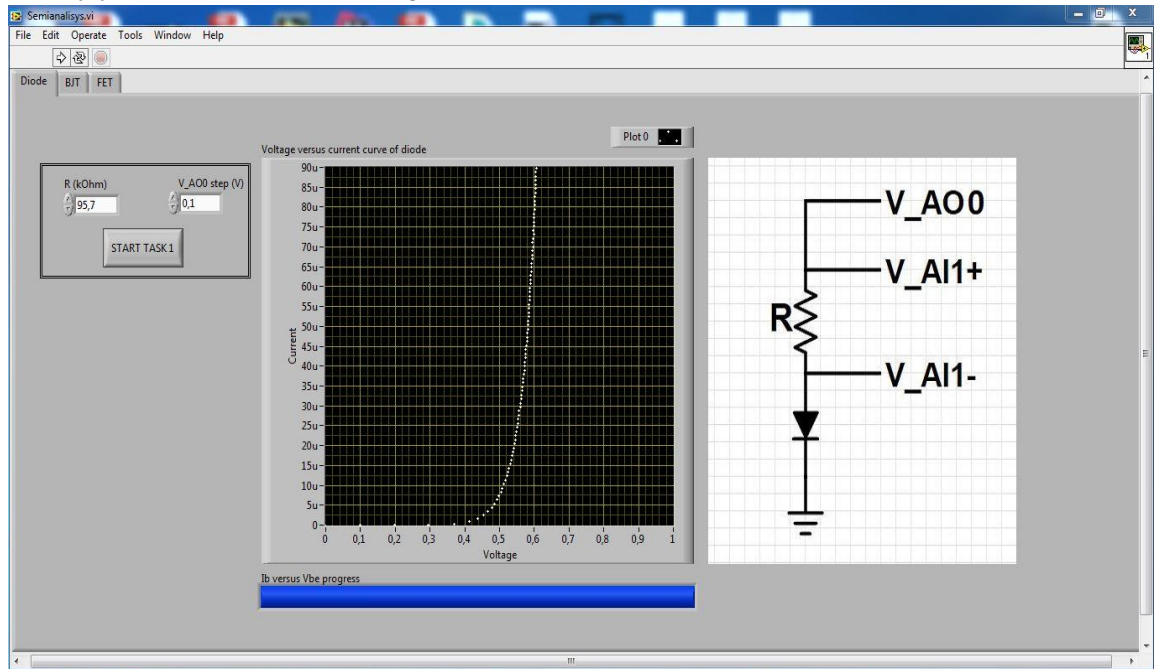

Task 2

BJT characteristics curves

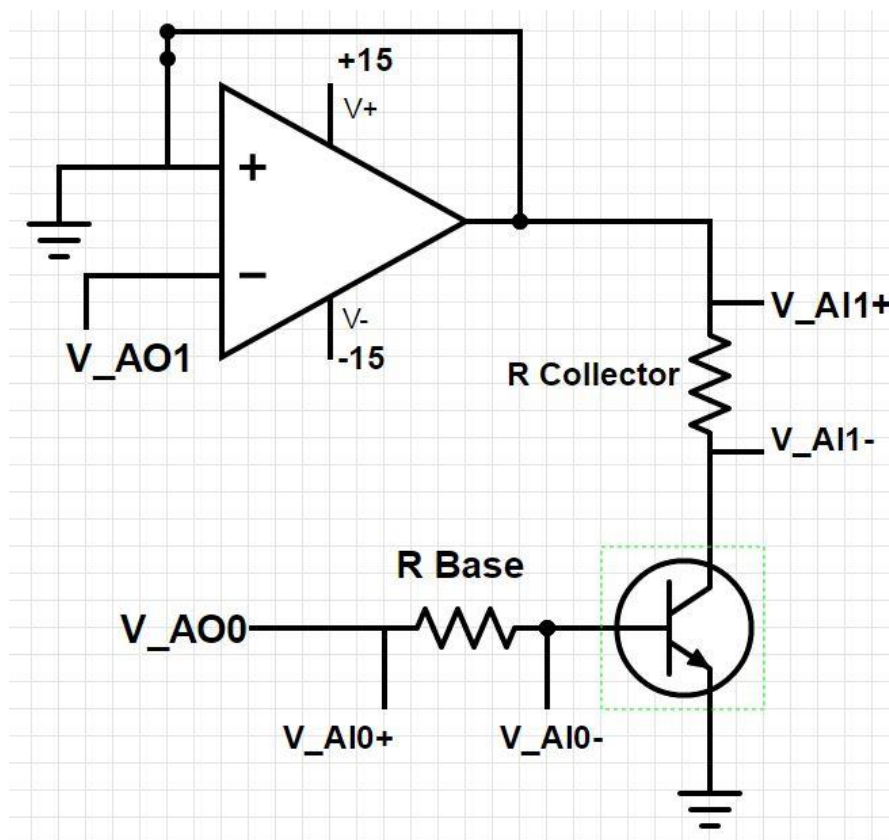



Figure 11. BJT circuit

To plot base current (I_B) versus base-emitter voltage (V_{BE}) graph V_{AO0} will be incrementing by steps that written in V_{be} step(V). NI myDAQ will read difference between $V_{AI} 0+$ and $V_{AI} 0-$ and divide by R which is our current through base. Each iteration will be putted on the graph and make first curve. For inverting pin of OP AMP analog output voltage(V_{AO1}) should be connected. For second curve V_{AO0} will be set by order written in application and hold while analog output (V_{AO1}) will be incrementing from 0 V to 10 V by step that you choose by putting V_{ce} step(V). Each iteration will be putted on the graph and make second curve.

1. Build the circuit as shown in Figure 11. $R_{base} = 1M\Omega$. $R_{collector} = 1k\Omega$. BJT(2N3904CN).
2. Connect to correct pins of NI myDAQ . Supply pins of OP AMP should be connected to +15V and -15V on NI myDAQ. Ground to AGND.
3. Measure R_{base} and $R_{collector}$ by using digital multimeter.
4. Open application and write founded value of resistors to R_{base} and $R_{collector}$.
5. Put 0.1 V for V_{be} step(V) and V_{ce} step(V).

6. Write number of curves 3 (you can choose from 1 to 8). Set appropriate three base current (I_B) values into the array.

7. Run the application.
8. Finally you should have something like this

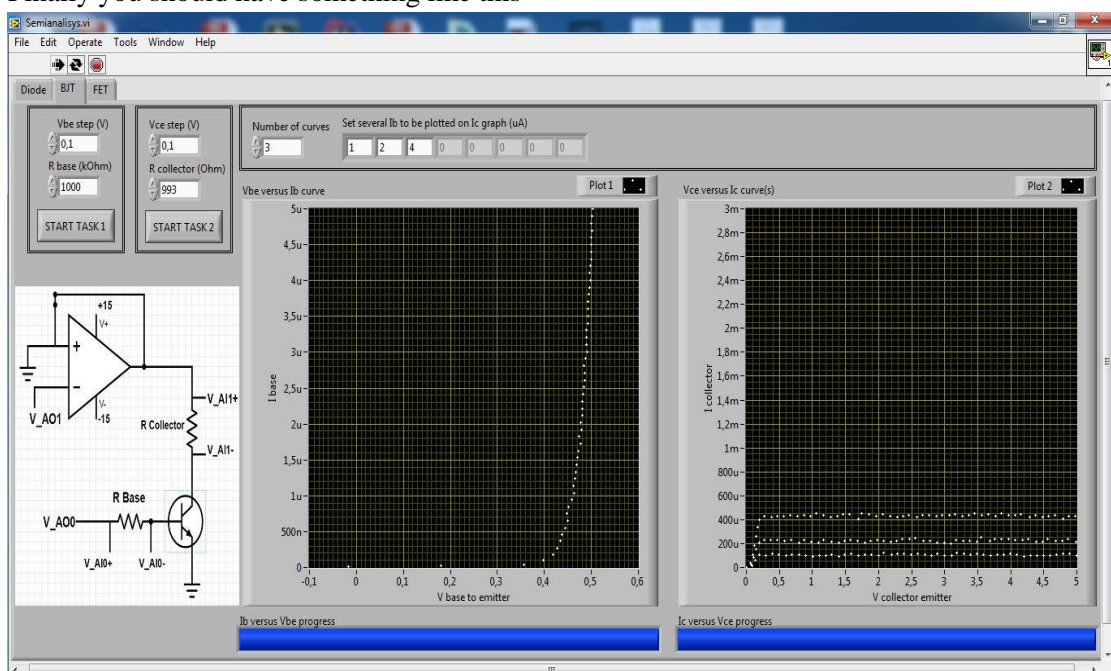

Task 3

JFET characteristics curves

Application will do same step as in BJT curve tracing. Only difference is that R_{gate} not important (because current through gate equal to 0). You can either put or remove R_{gate} .

To plot drain current (I_D) versus gate to source voltage (V_{GS}) graph V_{AO0} will be incrementing by steps that written in V_{gs} step(V). NI myDAQ will read difference between V_{AI1+} and V_{AI1-} and divide by R_{drain} which is our current through drain. Each iteration will be putted on the graph and make first curve. For inverting pin of OP AMP analog output voltage(V_{AO1}) should be connected.

For second curve V_{AO0} will be set by order written in application and hold while analog output (V_{AO1}) will be incrementing from 0 V to 10 V by step that you choose by putting V_{dc} step(V). Each iteration will be putted on the graph and make second curve.

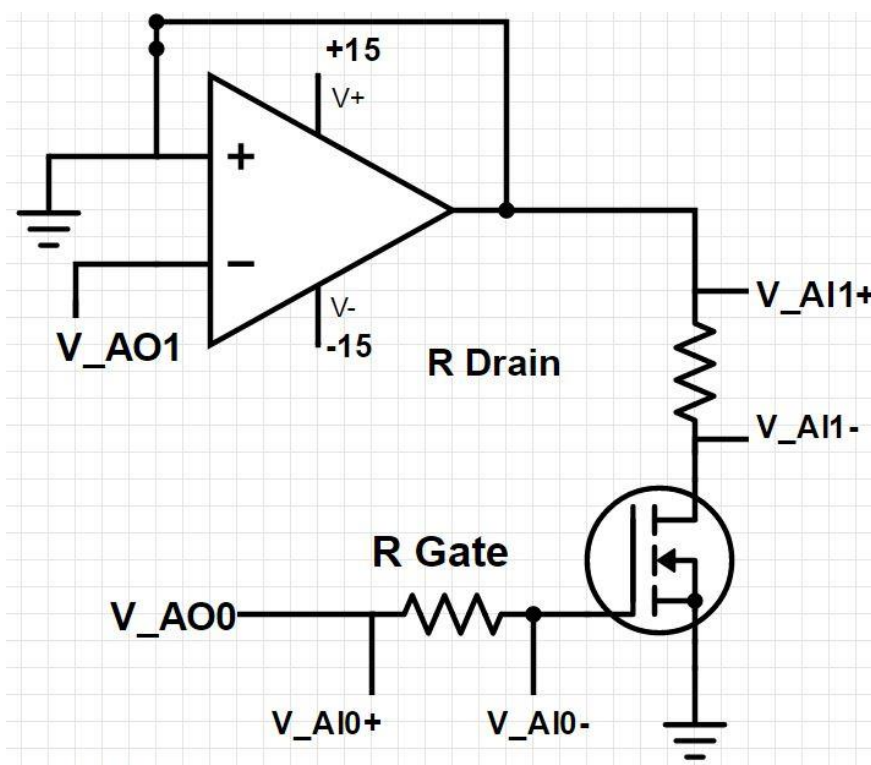


Figure 12. JFET circuit.

1. Build the circuit as shown in Figure 11. $R_{collector} = 1k\Omega$. JFET(2N5457).
2. Connect to correct pins of NI myDAQ . Supply pins of OP AMP should be connected to +15V and -15V on NI myDAQ. Ground to AGND.
3. Measure R_{drain} by using digital multimeter.
4. Open application and choose JFET(you can choose from JFET, DMOSFET or EMOSFET) then write founded value of resistor to R_{drain} .


- Put 0.1 V for V_{GS} step(V) and V_{DS} step(V).

Type of FET <input type="text" value="JFET"/>	V_{DS} step (V) <input type="text" value="0,1"/>
V_{GS} step (V) <input type="text" value="0,1"/>	R drain (Ohm) <input type="text" value="993"/>
<input type="button" value="START TASK 1"/>	<input type="button" value="START TASK 2"/>

- Write number of curves 3 (you can choose from 1 to 8). Set appropriate three voltage (V_{GS}) values into the array.

Number of curves <input type="text" value="3"/>	Set several V_{GS} to be plotted on V_{DS} graph (V) <input type="text" value="-1,5"/> <input type="text" value="-1"/> <input type="text" value="0"/> <input type="text" value="0"/> <input type="text" value="0"/> <input type="text" value="0"/> <input type="text" value="0"/> <input type="text" value="0"/>
--	---

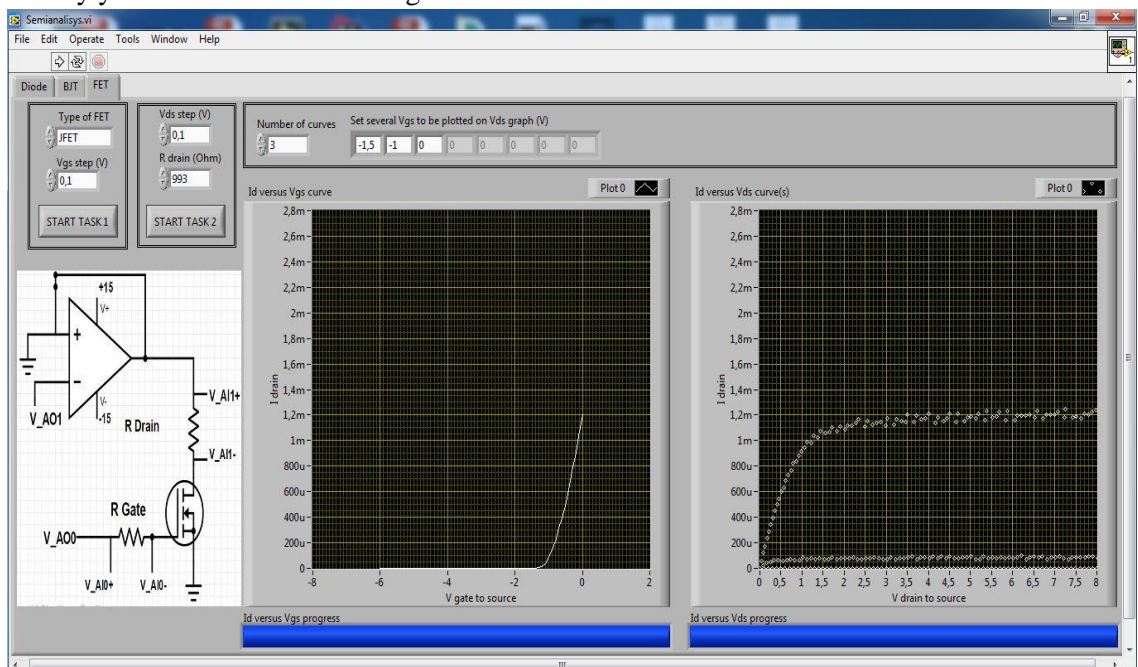- Run the application.
- Finally you should have something like this



- Repeat same process for DMOSFET.

References:

- "JFET-Junction Field Effect Transistor." *Electronic Circuits and Diagram Electronics Projects and Design*. N.p., 12 Nov. 2013. Web. 03 May 2016.
<http://www.circuitstoday.com/jfet-junction-field-effect-transistor>
- Boylestad, Robert L., and Louis Nashelsky. *Electronic Devices and Circuit Theory*. Upper Saddle River, NJ: Prentice Hall, 2014.